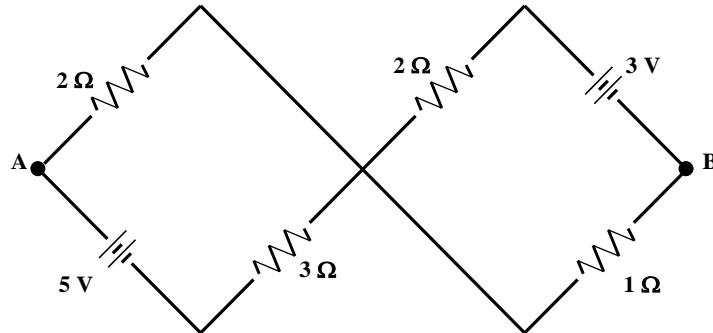


## Basic Electrical Engineering (ELE 1051)

### Test- 01

#### Scheme of Evaluation

- 1 A heater coil made of **Nichrome wire** is of rating 2000 W is cut in to two equal halves. If it is now connected in parallel and used, what would be its wattage?  
A. 2000 W    B. 500 W    C. 4000 W    D. **8000 W**
- 2 For the circuit shown below, find  $V_{AB}$ .




- A. **3 V**    B. 2 V    C. - 2 V    D. - 3 V
- 3 For the network equation given, Identify the pair of loops without common branch.

$$\begin{bmatrix} 50 & -10 & -15 & -20 \\ -10 & 60 & -5 & -25 \\ -15 & -5 & 40 & 0 \\ -20 & -25 & 0 & 70 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

- A. 2 and 3    B. **3 and 4**    C. 2 and 4    D. 1 and 4
- 4 For the network equation given, find the value of resistance connected between node 3 and reference node.


$$\begin{bmatrix} 0.29 & -0.05 & 0 & -0.2 \\ -0.05 & 0.175 & -0.025 & -0.1 \\ 0 & -0.025 & 0.295 & -0.25 \\ -0.2 & -0.1 & -0.25 & 1.05 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} -2 \\ 2 \\ 3 \\ 5 \end{bmatrix}$$

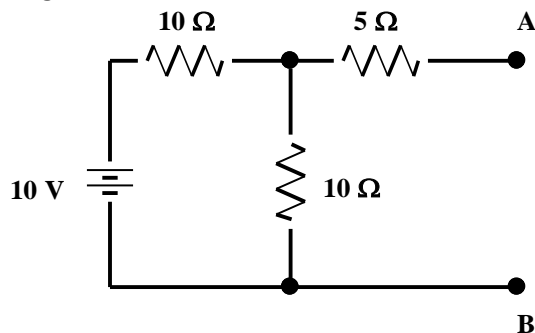- A. 40 Ω    B. 20 Ω    C. **50 Ω**    D. 25 Ω
- 5 Thevinin equivalent of the circuit given has  $V_{TH}$  and  $R_{TH}$



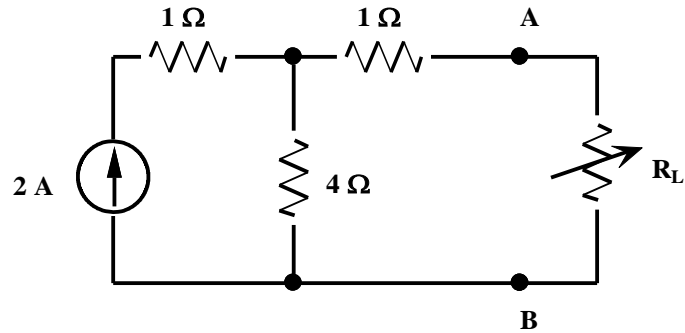- A. **5 V and 10 Ω**    B. 10 V and 10 Ω    C. 5 V and 5 Ω    D. 10 V and 5 Ω

- 6 In the circuit given, if the load resistance  $R_L$  can take any positive value, the maximum power transferred to load would be




- A. 3 W      B. 3.16 W      C. **3.2 W**      D. 4 W

- 7 An RC series circuit with  $R = 100 \Omega$  and  $C = 100 \mu\text{F}$  is switched across a DC voltage source of 12 V. If initial rate of rise of voltage is maintained, find the time taken for the voltage across capacitor to reach 6 V. Assume the capacitor is initially relaxed.

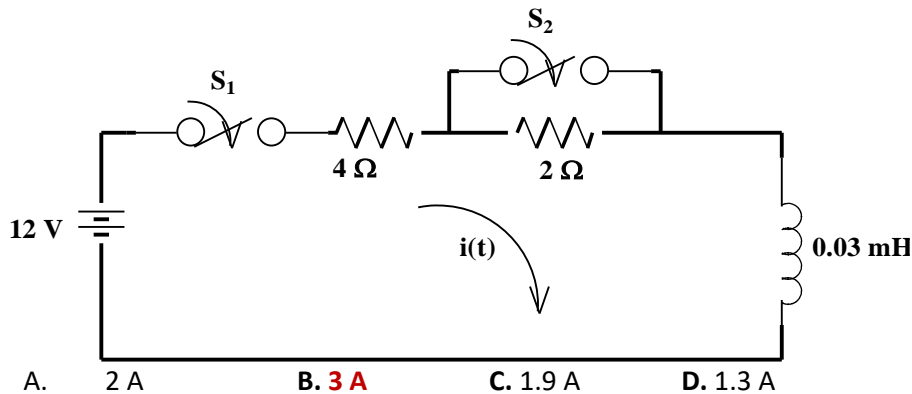- A. 10 ms      B. 6.93 ms      C. 13.86 ms      D. **5 ms**

- 8 In the RL circuit given if the switch  $s_1$  is closed at time  $t = 0$  second and the switch  $s_2$  is closed at time  $t = 5$  millisecond. Find the final value of current flowing through the inductor.



- A. 2 A      B. **3 A**      C. 1.9 A      D. 1.3 A


- 9 Equivalent of **Resistivity** in magnetic circuit is


- A. Permeability      B. Permeance      C. Reluctance      D. **Reciprocal of Permeability**

- 10 Equivalent of Permeance in Electric circuit is

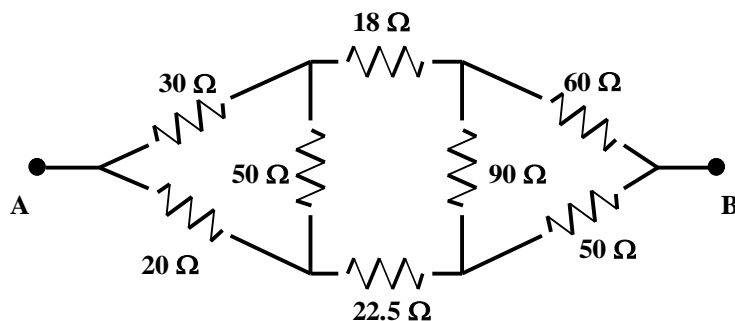- A. Resistance      B. Resistivity      C. Temperature coefficient of Resistance      D. **Conductance**

- 11 Find the equivalent resistance between terminals A & B.




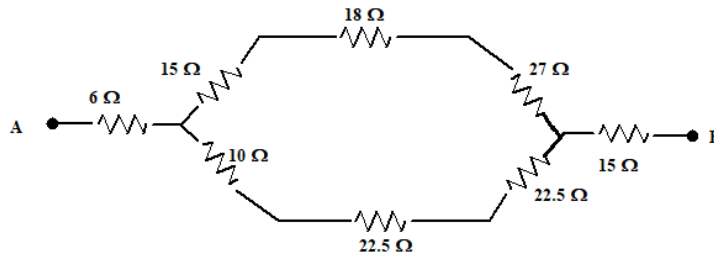


-----1Mark

$$R_{AB} = 49.7 \Omega$$

-----1Mark

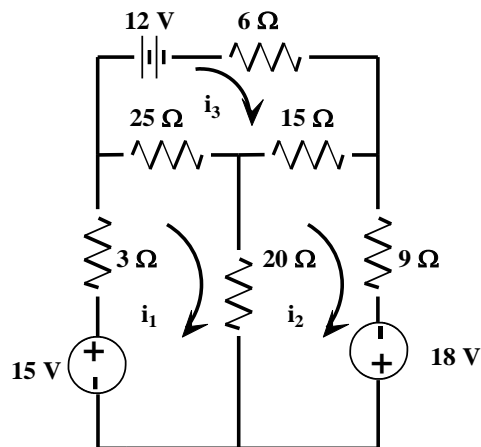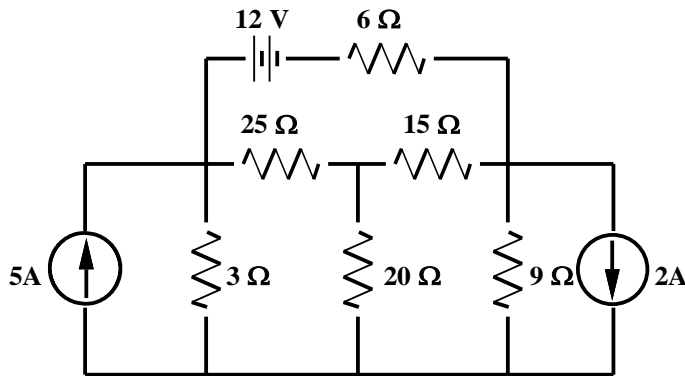- 12 Write the mesh equations of the network given and express in matrix form.




-----1Mark

$$\begin{bmatrix} 48 & -20 & -25 \\ -20 & 44 & -15 \\ -25 & -15 & 46 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 15 \\ 18 \\ -12 \end{bmatrix}$$

-----1Mark

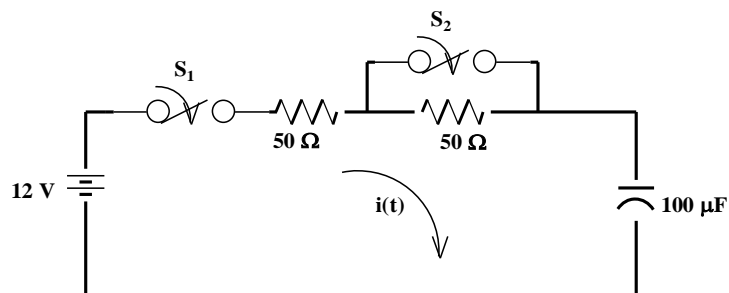- 13 In the RC circuit given if the switch  $s_1$  is closed at time  $t = 0$  second and the switch  $s_2$  is closed at time  $t = 5$  millisecond. Find the time taken for the capacitor to get charged to 8 V.



$$v_c(t) = V_s \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$v_c(t) = 4.7216 \text{ V}$$


---- 1Mark

$$v_c(t) = V_s - (V_s - V_o) \left(1 - e^{-\frac{(t-t_0)}{\tau}}\right)$$

$$t = 8 \text{ ms}$$

---- 1Mark

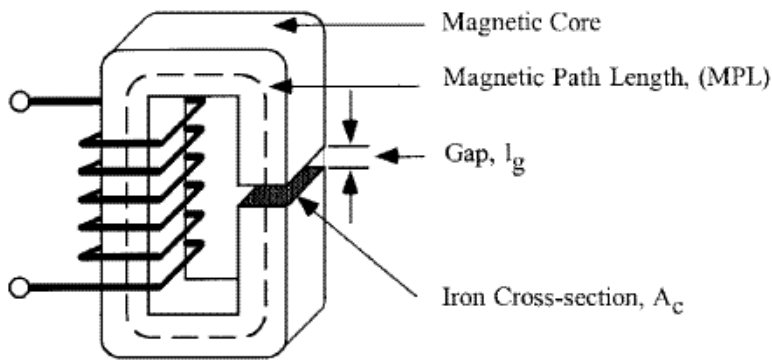- 14 Find the number of turns of the coil required to drive a flux of 0.0002 Wb in the ferromagnetic core shown in the figure. Given current through the coil 5A, MPL = 30 cm,  $l_g = 1 \text{ mm}$ ,  $A_c = 2 \text{ cm}^2$ ,  $\mu_r = 2000$




$$NI = \phi(S_f + S_{ag})$$

----1Mark

$$N = \frac{0.2m \left( \frac{0.3}{\mu_o \times 2000 \times 2 \times 10^{-4}} + \frac{1m}{\mu_o \times 2 \times 10^{-4}} \right)}{5} = 183 \text{ turns}$$

----1Mark

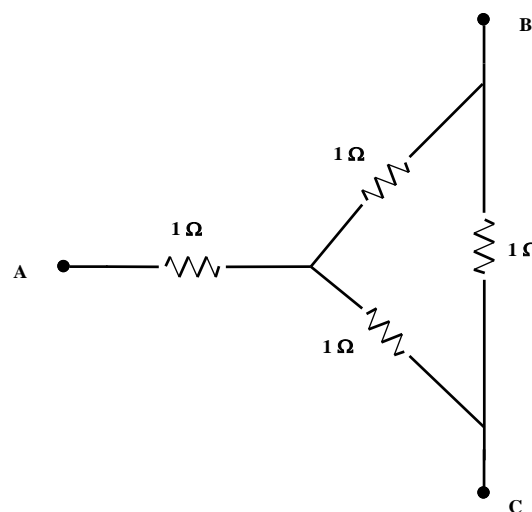- 15 Given a black box with three terminals, as shown below. The box contains four 1-ohm resistors interconnected. Given the resistance measured between the two terminals are  $R_{AB} = 1.66\Omega$ ,  $R_{BC} = 0.66\Omega$ ,  $R_{AC} = 1.66\Omega$ . Realise the resistive network.



----2 Mark