
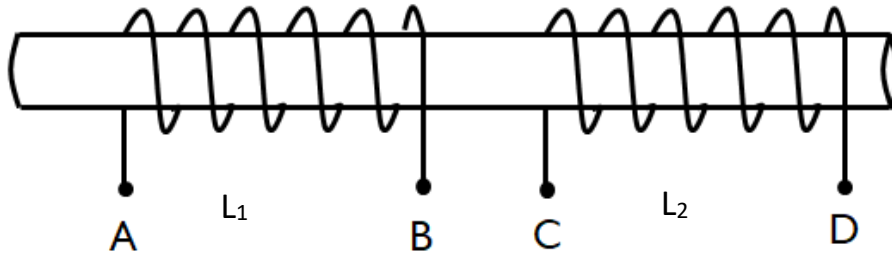


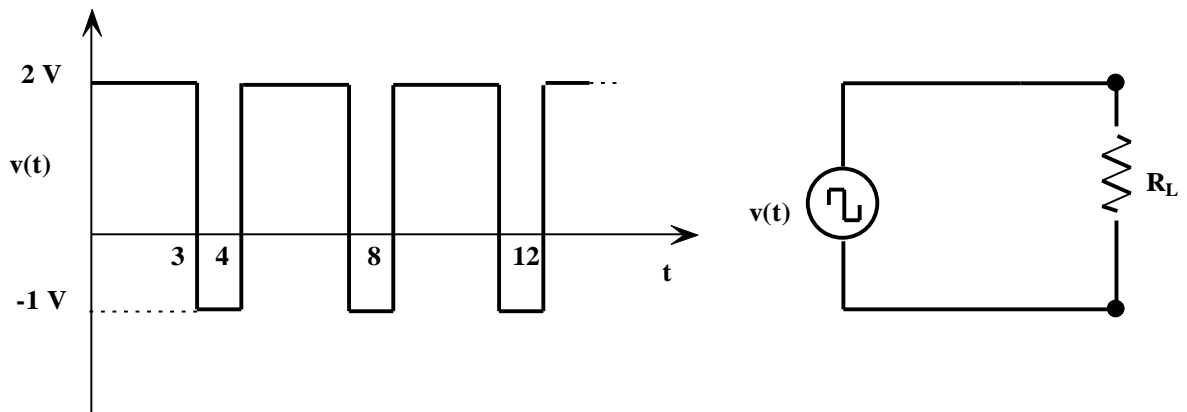
- Q. No. 1 Magnetically coupled circuit shown in the figure has $L_1 = 4.5 \text{ H}$, $L_2 = 2 \text{ H}$, the coefficient of coupling 0.7 and the terminals B and D are connected. The equivalent inductance measured across A & C would be



- A) 10.7 H B) 8.6 H C) **2.3 H** D) 4.4 H
- Q. No. 2 Given voltages $v_1(t) = 339.4 \sin 314 t$ and $v_2(t) = 339.4 \cos 314 t$. The RMS value of $v_1(t) + v_2(t)$ would be
- A) 479.98 V B) **339.4 V** C) 277.13 V D) 240 V
- Q. No. 3 In the circuit given, find the value of the equivalent DC source voltage to produce the same heating effect in the load?




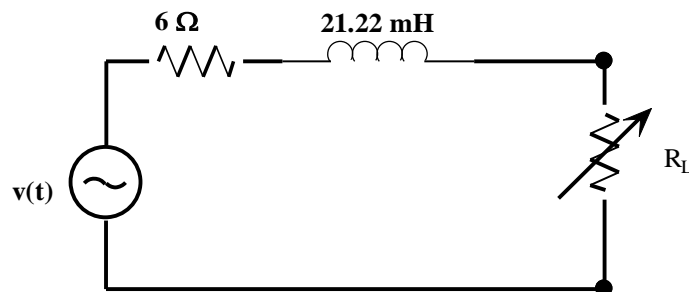- A) 1.5 V B) 1.732 V C) **1.8 V** D) 2.246 V
- Q. No. 4 In the circuit given $v(t) = 339.4 \sin 377 t$ and the load R_L is variable; find the maximum power drawn by the load?



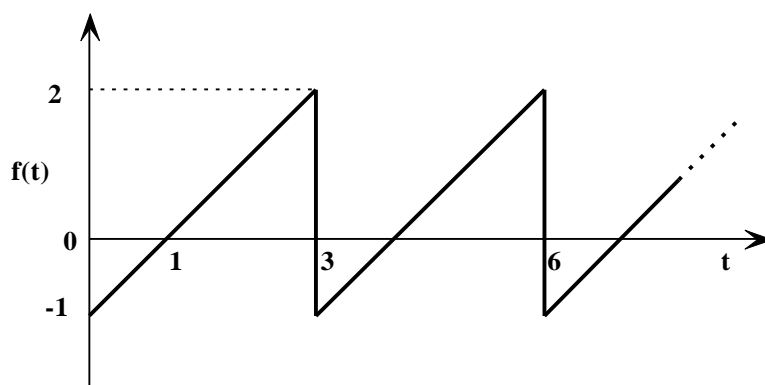- A) 2880 W B) 1440 W C) **1800 W** D) 3600 W
- Q. No. 5 An R L series circuit with $R = 5 \Omega$ and $L = 31.85 \text{ mH}$ is connected to an AC voltage source $v(t) = 339.4 \sin 377 t$. Find the expression for the current in the circuit.
- A) **$i(t) = 26.11 \sin(377 t - 67.38^\circ)$** C) $i(t) = 30.36 \sin(377 t - 63.44^\circ)$
 B) $i(t) = 30.36 \sin(377 t - 67.38^\circ)$ D) $i(t) = 26.11 \sin(377 t - 63.44^\circ)$

- Q. No. 6 Two loads $S_1 = 100 \text{ KVA}$ at 0.8 pf lagging and $S_2 = 100 \text{ KW}$ are operated together. What is the overall load power factor?
 A) **0.949 (lagging)** B) 0.832 (lagging) C) 0.932 (lagging) D) 0.849 (lagging)
- Q. No. 7 A series RLC circuit, connected to a variable frequency voltage source, behaves like an inductive circuit with source frequency, f . The circuit can be brought to resonance by
 A) Increasing the supply frequency C) Increasing the value of Capacitance
 B) Increasing the value of Inductance D) **Decreasing the supply frequency**
- Q. No. 8 A parallel circuit with an RL series branch ($R = 10 \Omega$ and $L = 50 \text{ mH}$) and an RC series branch ($R = 10 \Omega$ and $C = 100 \mu\text{F}$) are connected to a variable frequency voltage source. Find at what frequency the circuit resonates?
 A) 447.21 Hz B) 223.61 Hz C) 142.35 Hz D) **71.18 Hz**
- Q. No. 9 In a 3 phase, 4 wire, 415 V, 50 Hz, balanced, RYB system; if the phasor $\mathbf{V}_{YB} = 415 \angle 0^\circ$ the phasor \mathbf{V}_{RN} will be
 A) **$240 \angle 90^\circ$** B) $240 \angle 120^\circ$ C) $240 \angle 60^\circ$ D) $240 \angle -90^\circ$
- Q. No. 10 In a 3 phase, 415 V, 50 Hz, balanced, RYB system; the instantaneous value of V_{RY} is measured as 586.9 V. Find the instantaneous value of V_{YB} at the same instant.
 A) 293.45 V B) **-293.45 V** C) -508.27 V D) 508.27 V
- Q. No. 11 Differentiate a *vector* and a *phasor*
 Vector : it has magnitude & direction
 Phasors: it's a representation of set of sinusoidally varying quantity of same frequency with its magnitude as RMS value & relative position as angle.
- Q. No. 12 Find the average value and effective value (RMS) of the saw tooth wave form shown




RMS Value : 1.19 V 1 Mark

Avg. Value : 0.5 V 1 Mark

- Q. No. 13 A 3 phase, 3 wire, 110 V, ABC system supplies a delta connected load of three equal impedances of $5 \angle 45^\circ \Omega$. Taking \mathbf{V}_{AB} as reference, find the value of line currents I_A, I_B, I_C
 $I_{AB} = 22 \angle -45^\circ \text{ A}$
 $I_{BC} = 22 \angle -165^\circ \text{ A}$
 $I_{CA} = 22 \angle 45^\circ \text{ A}$ **phase currents** 1 Mark
- $I_A = 38.11 \angle -75^\circ \text{ A}$
 $I_B = 38.11 \angle 165^\circ \text{ A}$
 $I_C = 38.11 \angle 45^\circ \text{ A}$ **line currents** 1 Mark

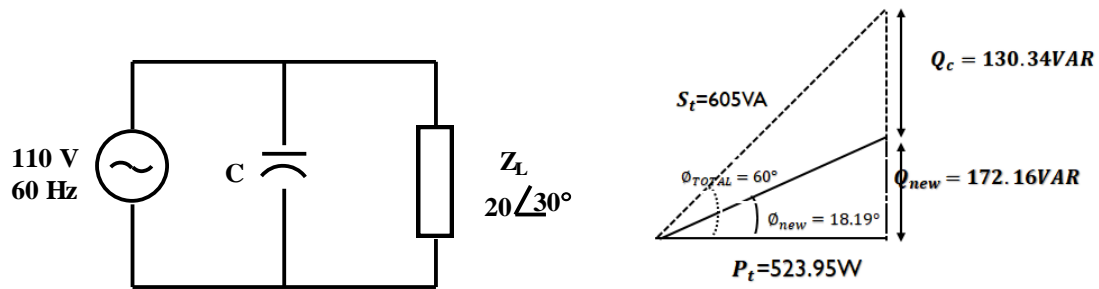- Q. No. 14 In the parallel circuit shown, Find the value of Capacitance C, necessary to correct the power factor to 0.95 lagging



$$P = 523.95 \text{ W}$$


$$Q = 302.5 \text{ VAR}$$

$$S = 605 \text{ VA} \text{-----1 MARK}$$

$$X_C = 92.84 \Omega$$

$$C = 28.57 \mu\text{F} \text{-----1 MARK}$$

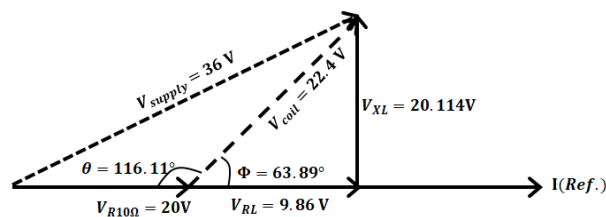- Q. No. 15 A coil of resistance R and inductance L is connected in series with a 10 Ω resistor and an AC sinusoidal voltage of 36 V, 60 Hz is applied across it. Find the value of R & L if the voltage across the 10 Ω resistor is 20 V and that across the coil is 22.4 V



$$\cos\theta = \frac{20^2 + 22.4^2 - 36^2}{2 \times 20 \times 22.4} = -0.44 \text{-----1 MARK}$$

$$\Phi = 180^\circ - 116.11 = 63.89^\circ$$

$$V_{RL} = 22.4 \cos(63.89) = 9.86 \text{ V} \Rightarrow R = 4.93 \Omega$$

$$V_{XL} = 22.4 \sin(63.89) = 20.114 \text{ V} \Rightarrow X_L = 10.06 \Omega \Rightarrow L = 26.68 \text{ mH}$$

$$\text{-----1 MARK}$$